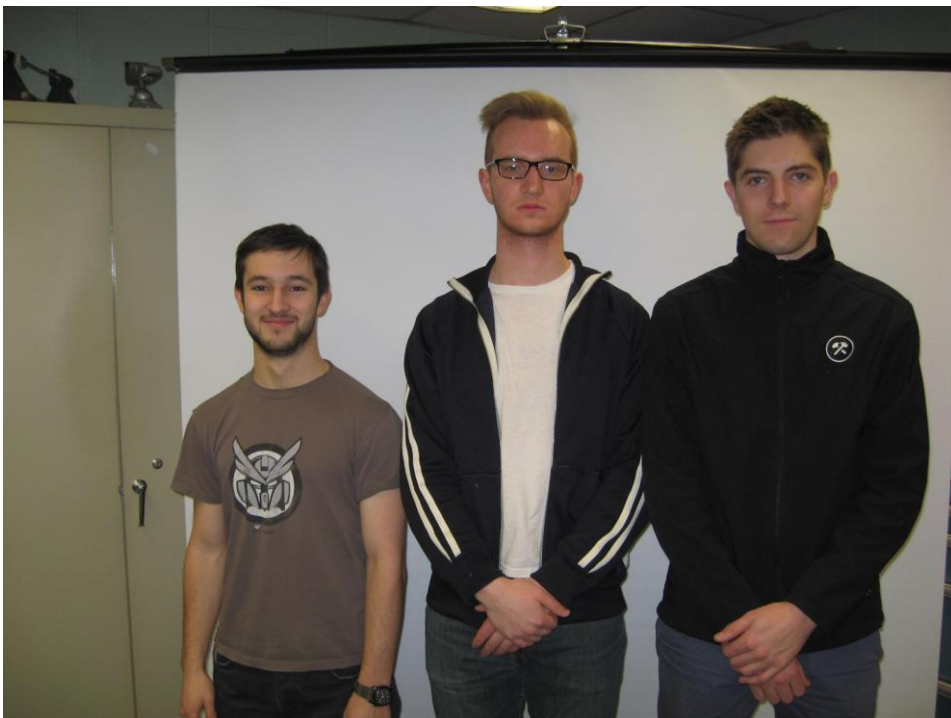



ECE 477 Design Review

Team15 – Social Lock

Team



System Block Diagram

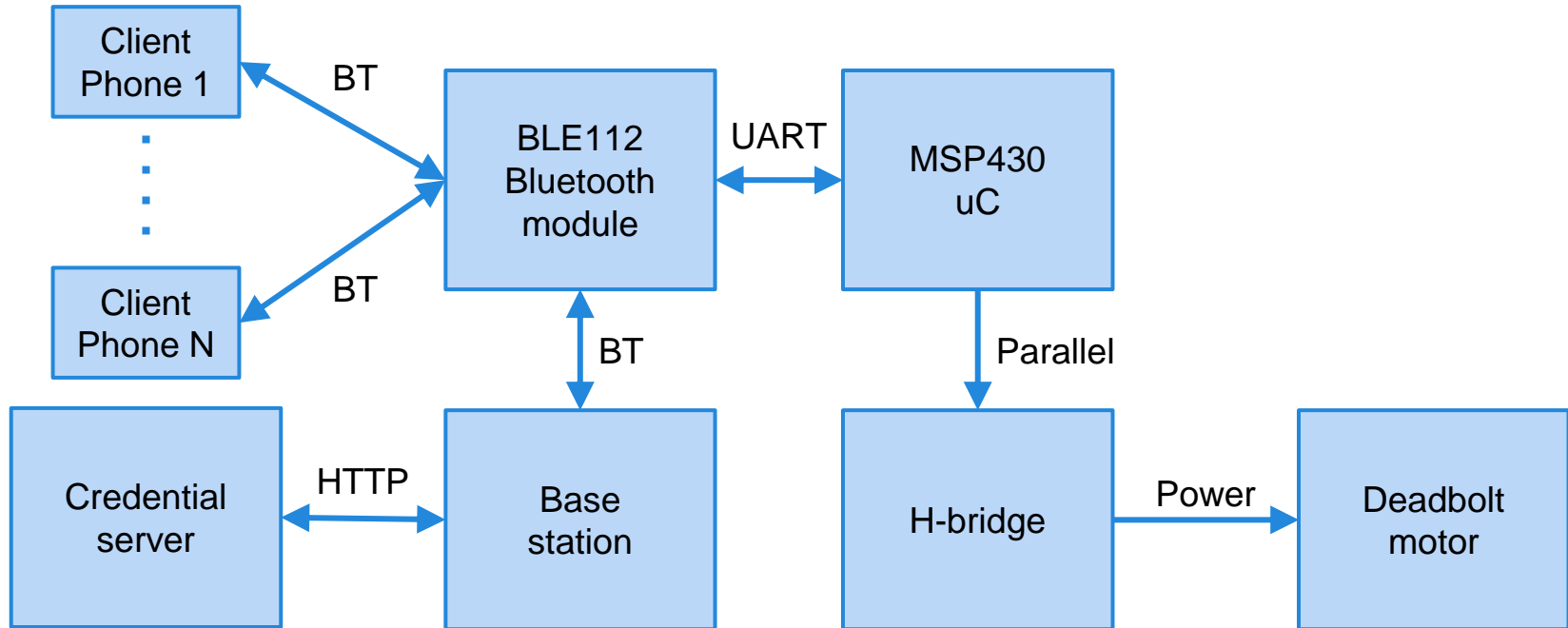

PSSCs

1. An ability to securely determine whether a given mobile device is authorized to unlock the door.
2. An ability to mechanically displace the deadbolt to unlock and relock the door.
3. An ability to monitor the battery state and indicate a low battery condition to the user.
4. An ability to grant and revoke access to additional smartphones without either being physically present at the lock.
5. An ability to use grant temporary access to additional smartphones which expires automatically at the appointed time.

Component Selection Rationale

Microcontroller

Bluetooth Module

H Bridge

LDO Regulator

Battery Monitor

Microcontroller

TI MSP430F6659

Strong Community
Powerful
Our team is familiar
with the tools



Bluetooth Module

Bluegiga BLE112

Built in
microcontroller
UART
Programmable
Well-supported



H Bridge


Toshiba TB6593FNG

Low minimum motor
supply voltage ($< 3V$)

Low ambient current
draw

High current capacity
(1.2A)


Analog control

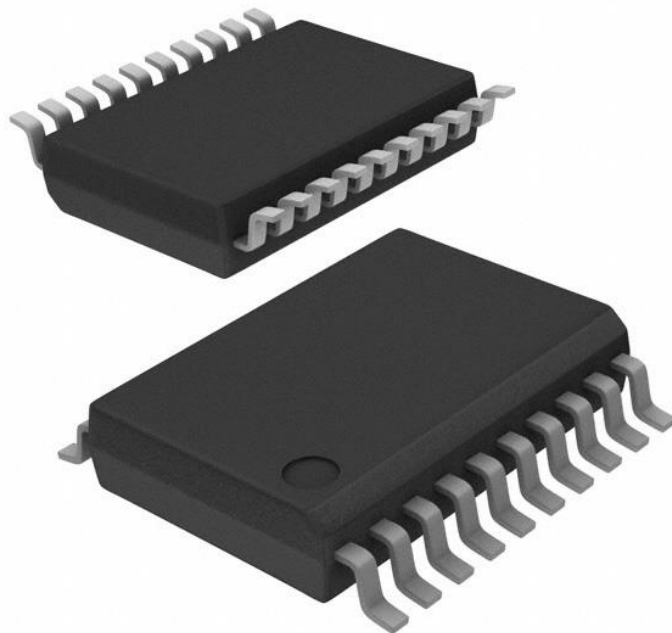

LDO Regulator

Microchip Technology MCP1700T

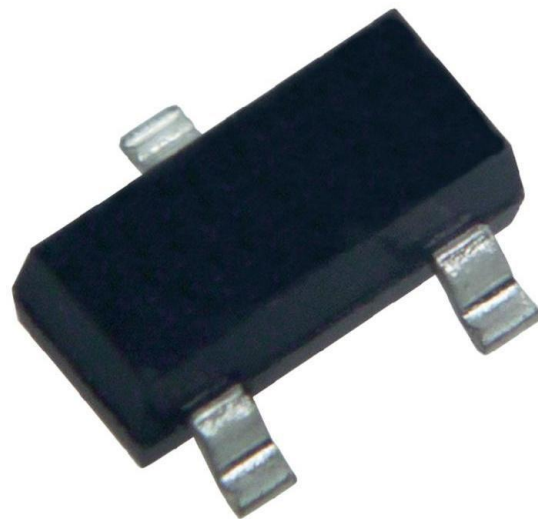Simple, 3 pin package
Max power consumption:
~150mW
Sleep power
consumption: ~15 uW



Battery Monitor

Maxim 6775XKA+T

Low, 0.87uA current draw

1% Accuracy


Only need to indicate low
battery warning

Simpler than coulomb counting



Packaging Design

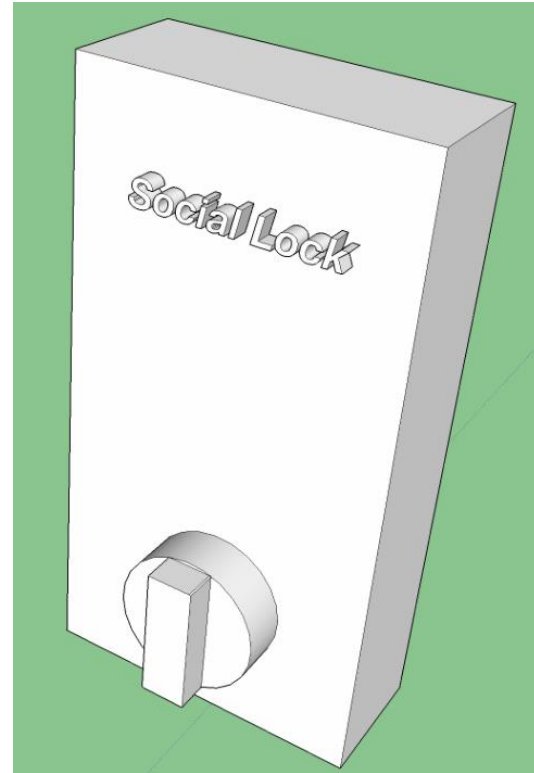
3D printed box that
fits over deadbolt
Does not require any
tools to install
Removable adhesive
affixes device to
door



Schematic broken
into blocks
Each block covered
in following slides




Power Block

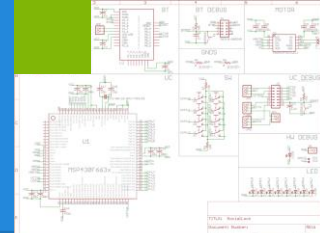


POWER

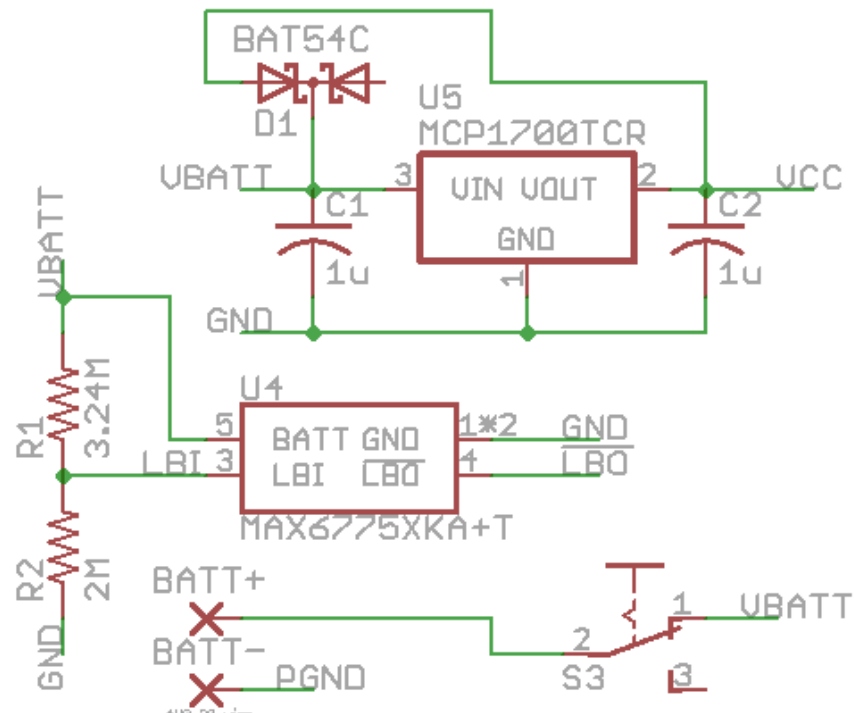
Battery leads
LDO regulator
Battery monitor
Power switch




Bluetooth Block

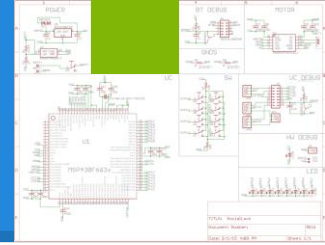

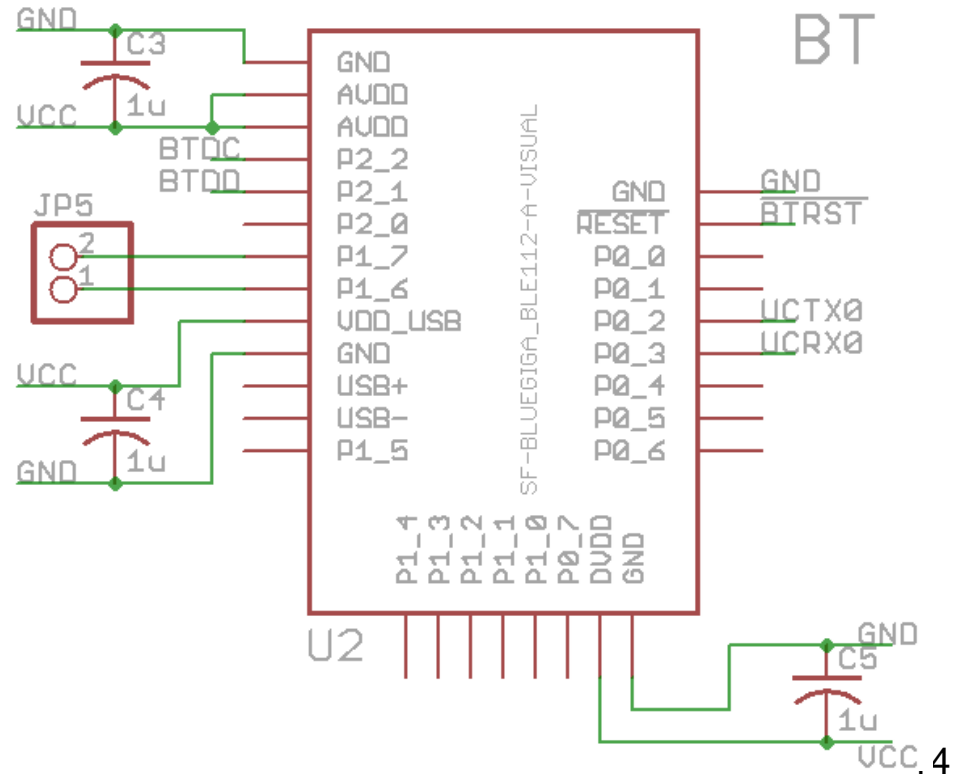
BLE112A module
Decoupling caps
uC UART
Debug UART




Bluetooth Debug Block

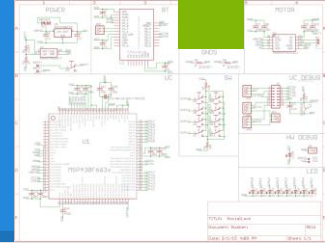

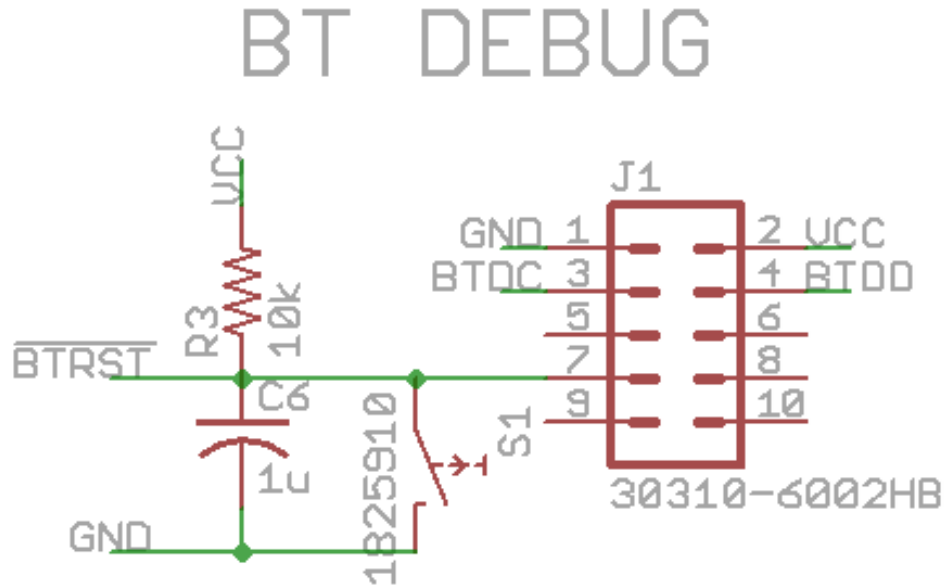10-pin JTAG
nRST switch
Vcc sense (not
supply)




Grounds Block

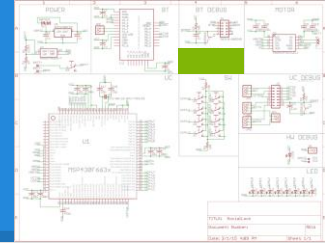

Fake resistors
Connect AGND,
PGND to GND

GNDs

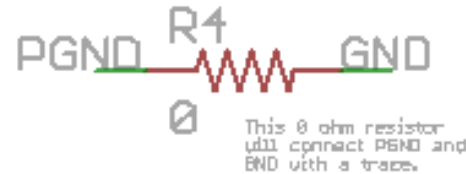

[illegible]


Decoupling caps

20-SSOP, 5 pins

Unregulated VBATT




uC Debug Block

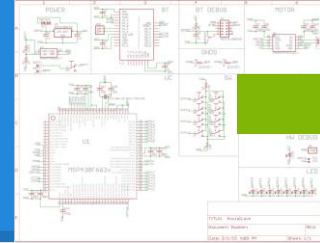


UC DEBUG

See 8LAU278U pp. 24, 161.

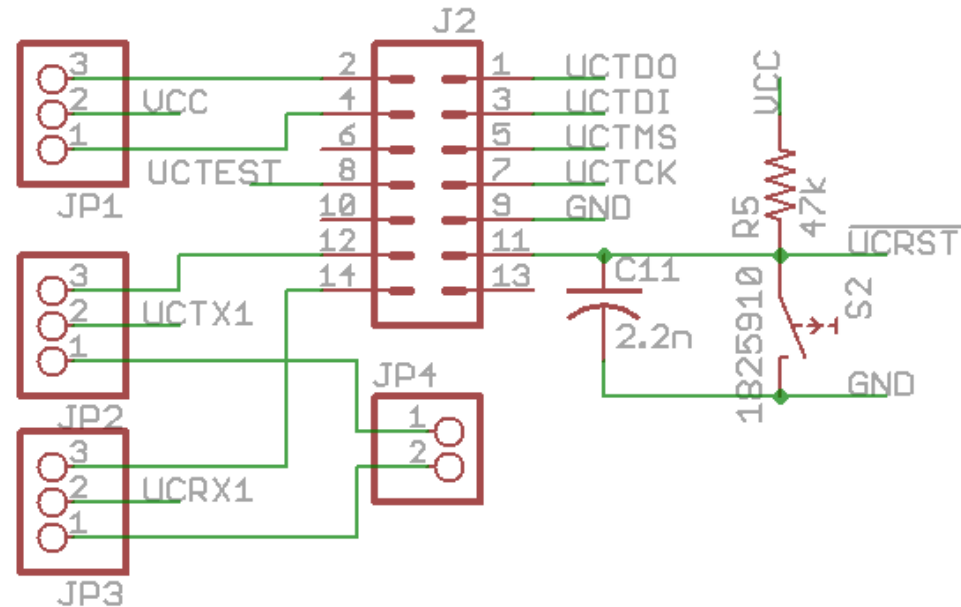14-pin JTAG
nRST shared with
debugger
Backchannel UART
Power source
selection





HW Debug Block

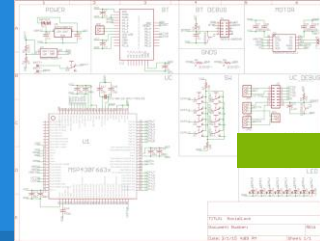


Power LED
Voltage test points


HW DEBUG

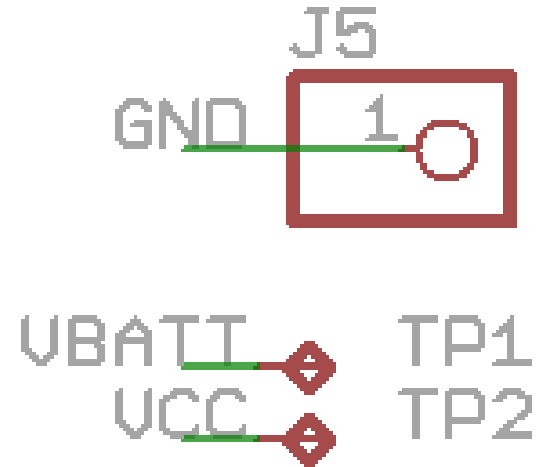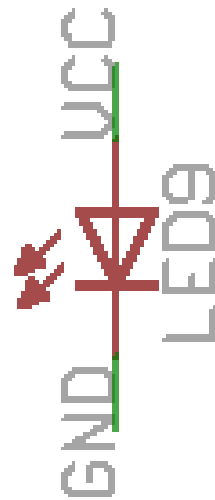


LED Block

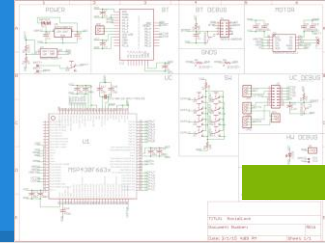


Output LEDs for uC

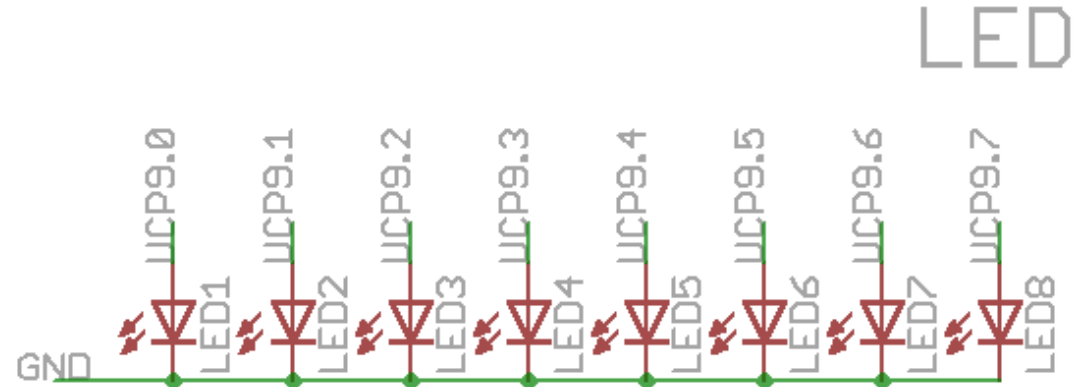

Switch Block

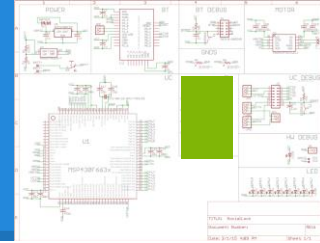


Input switches for uC

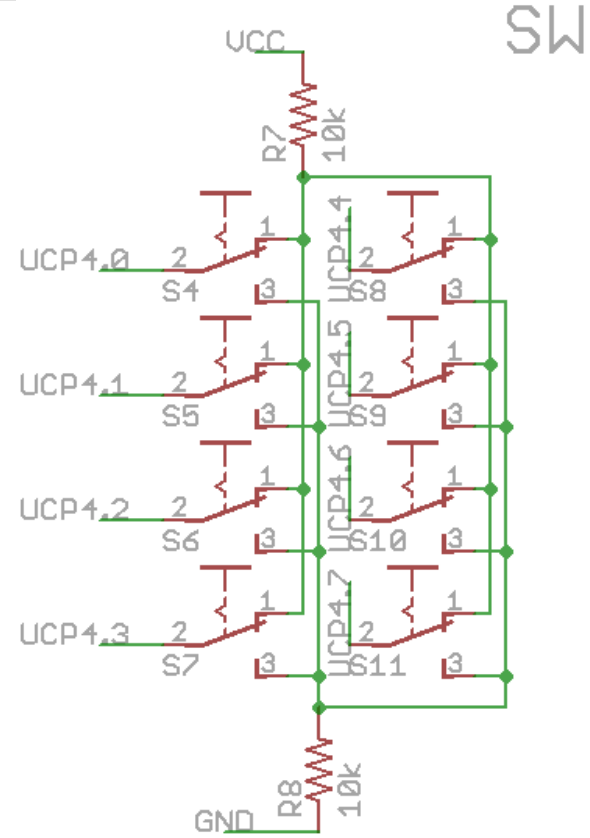


uC Block

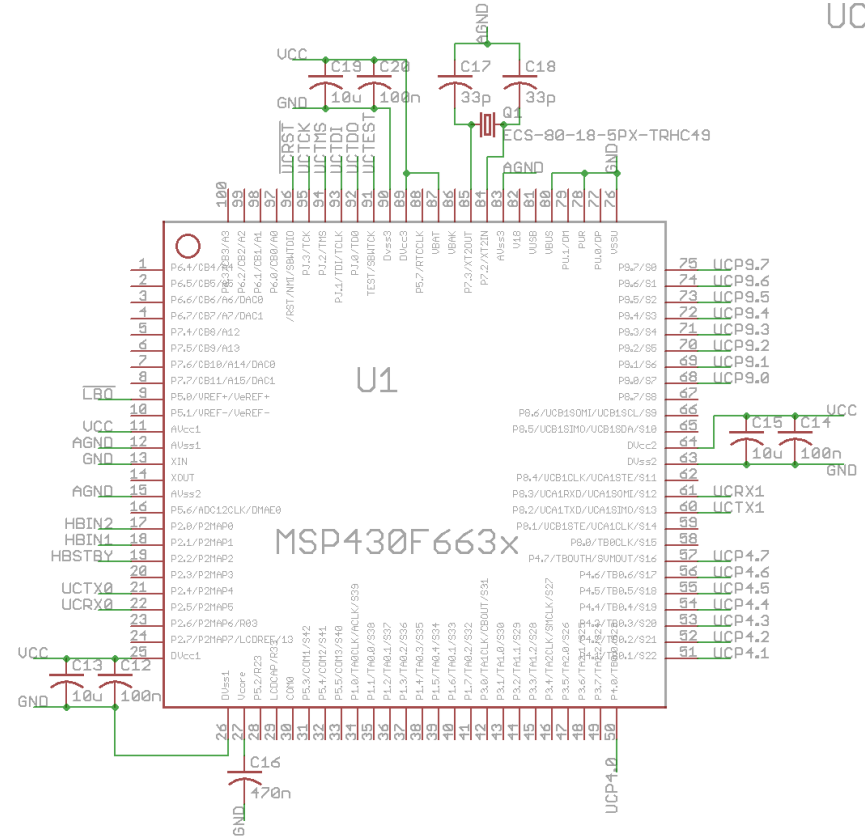
Isolated 8 MHz
crystal
Decoupling caps
Signal lines to
everything else




PCB Layout – 1.65"x3.95"

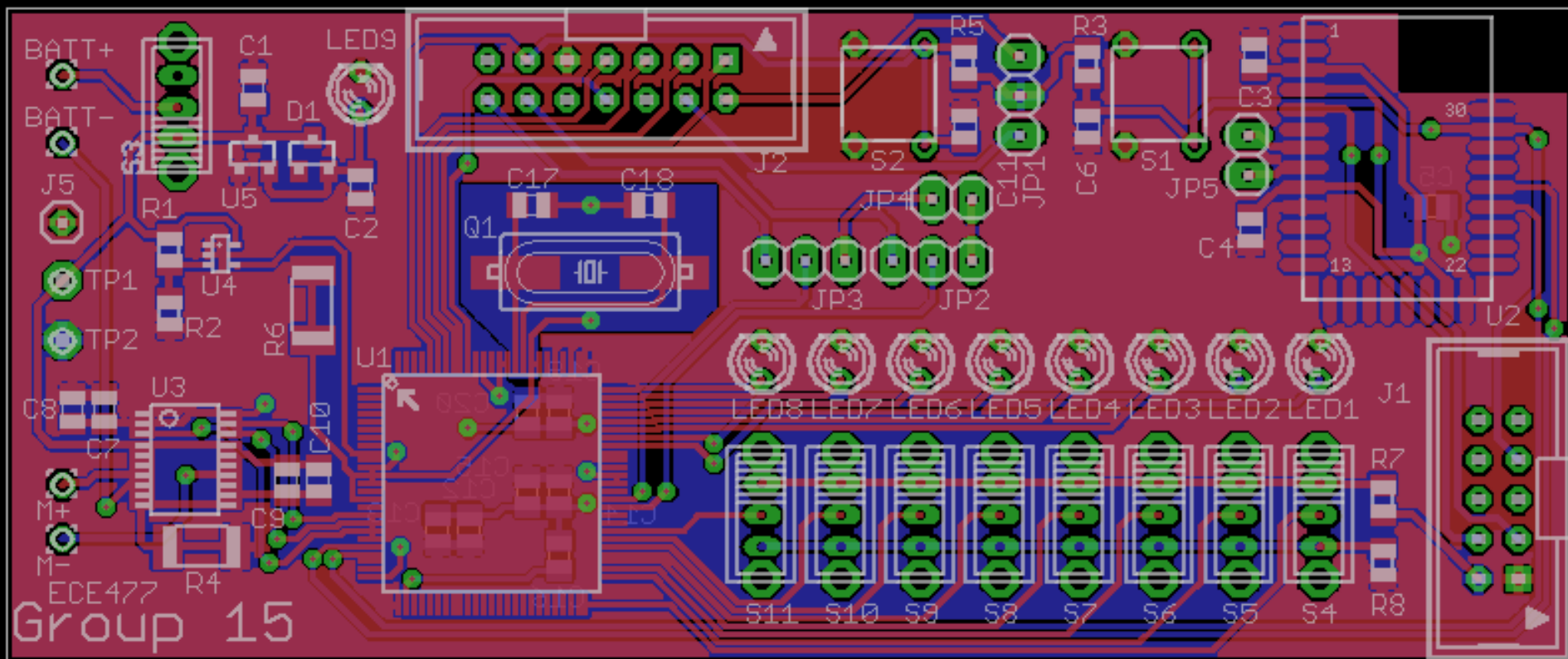


Power Layout

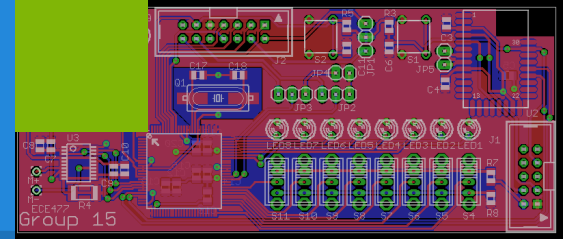

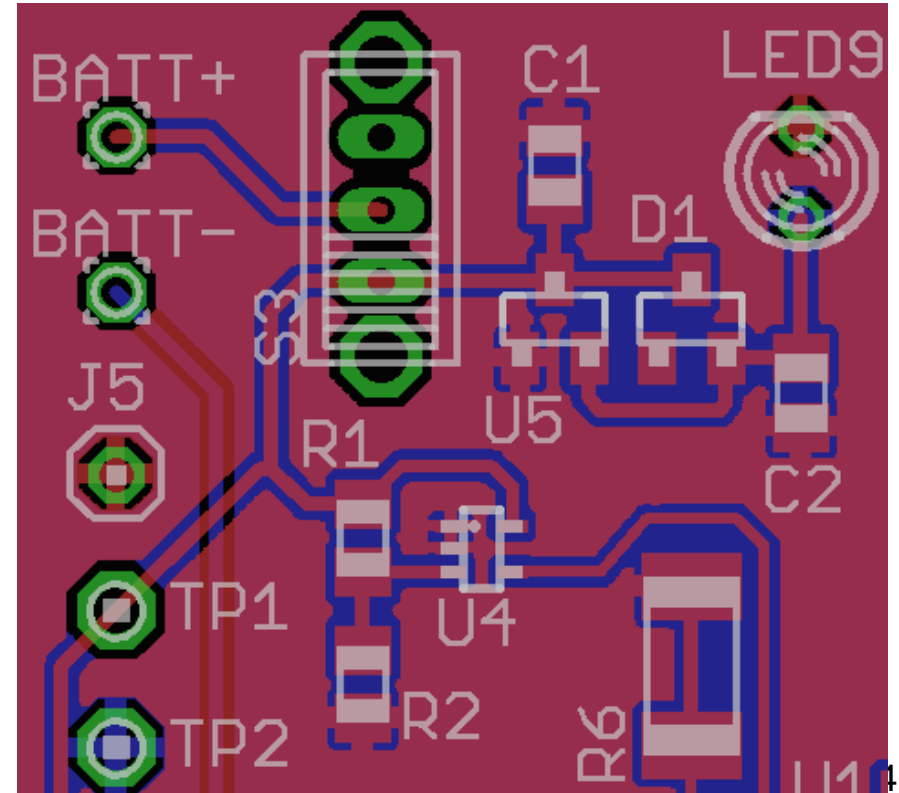
Power switch
Indicator LED
Back-voltage
protection via
Schottky diode



Motor Layout

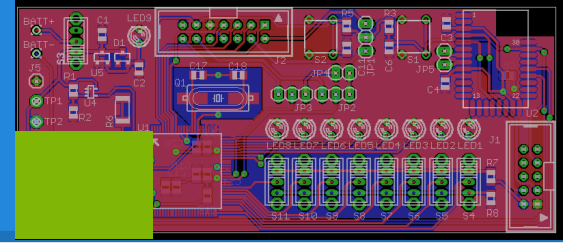


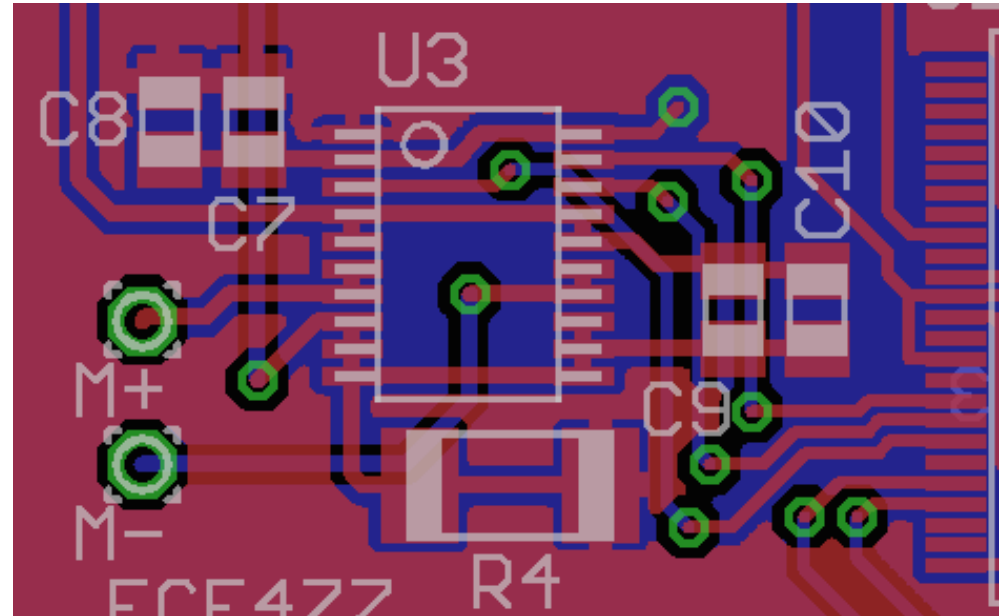
Pins inconveniently
configured
Most vias per pin of
all components
PGND connected to
GND at R4
uC at right




JTAG-14 Layout

Most difficult routing
Originally farther
from uC

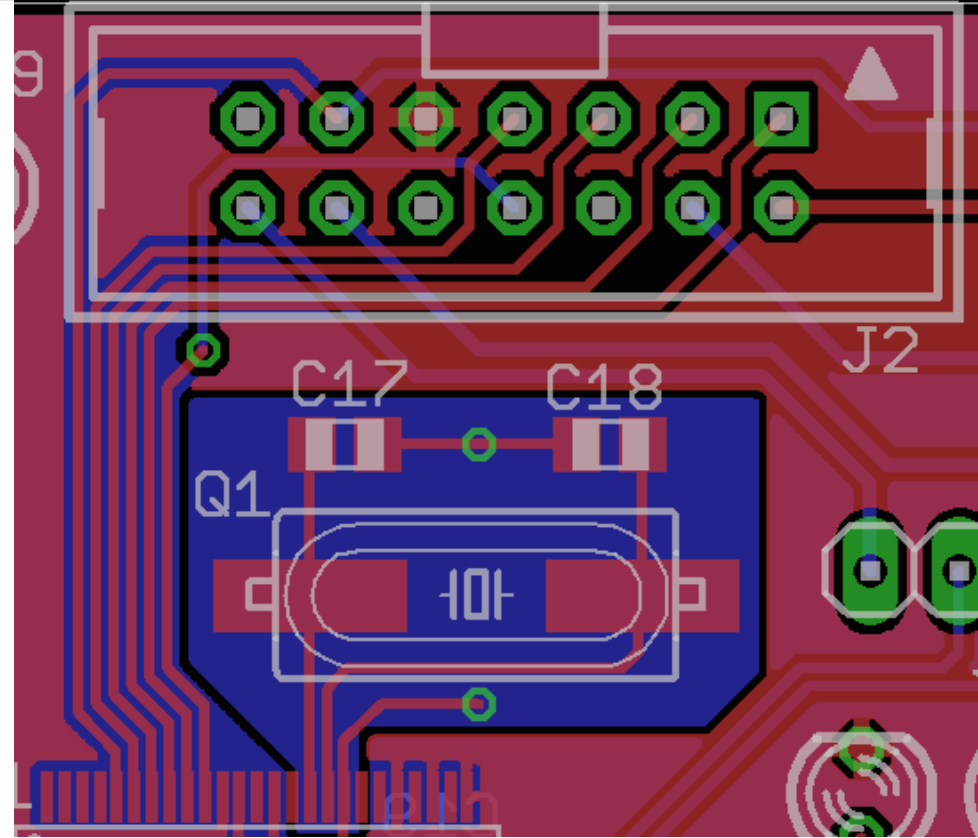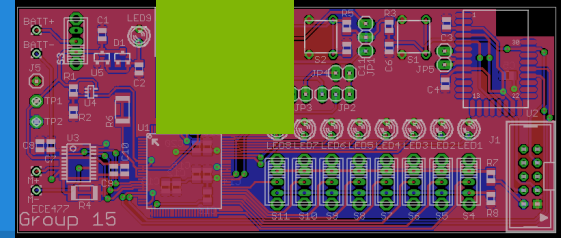
Solution: signals
from left on top;
from right, bottom




Jumper Layout

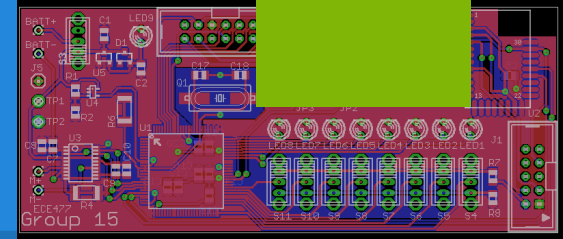

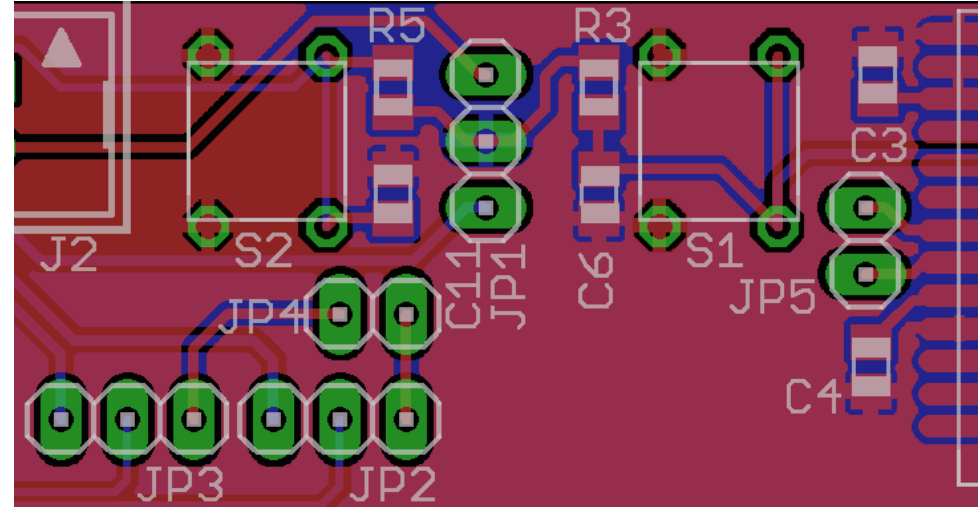
Allows selection of
uC UART path
Includes adjacent
nRST switches




Oscillator Layout

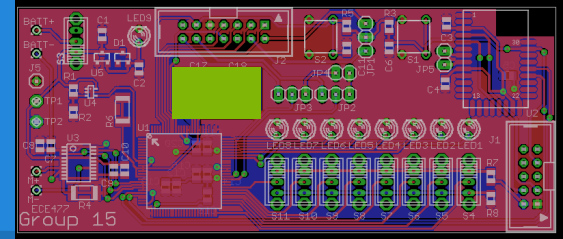

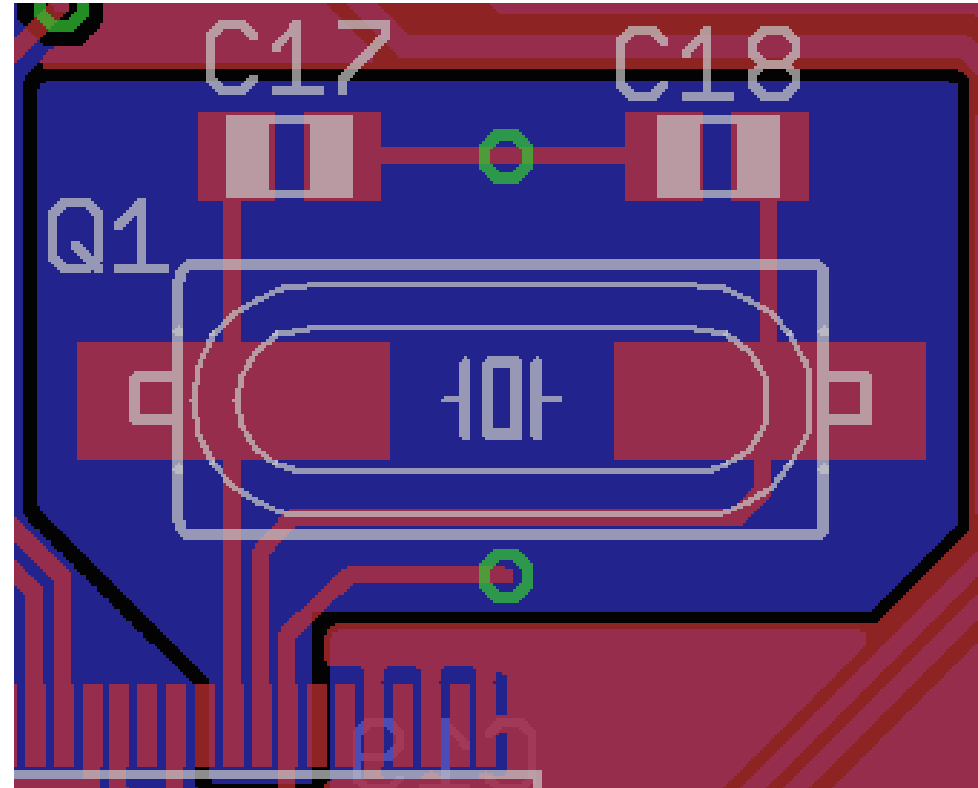
Analog circuit
Isolated analog
ground plane
Equal-length load
capacitor traces



Switch & LED Layout


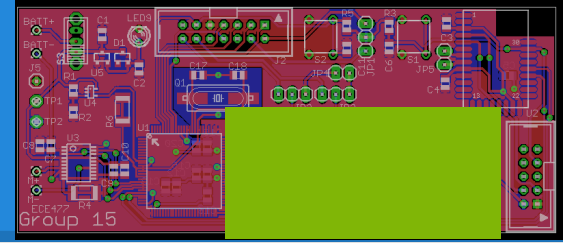


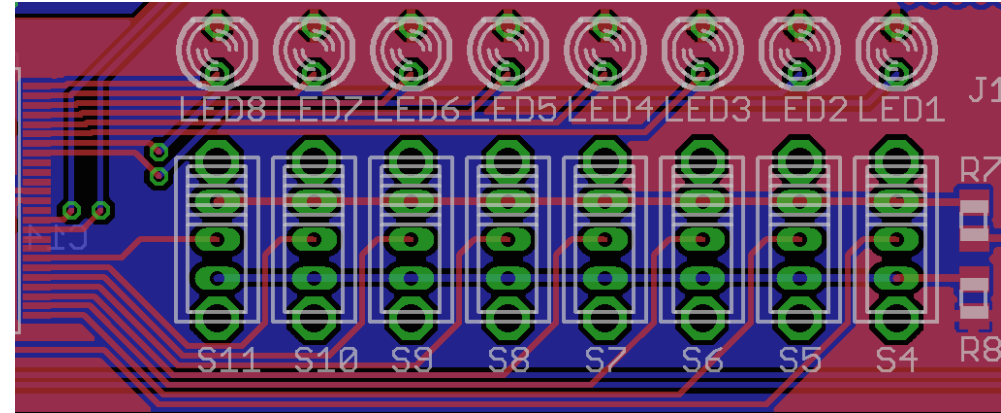8-bit I/O for
debugging
Switches include
PU/PD resistors for
safety




uC Layout

Decoupling caps on
bottom layer

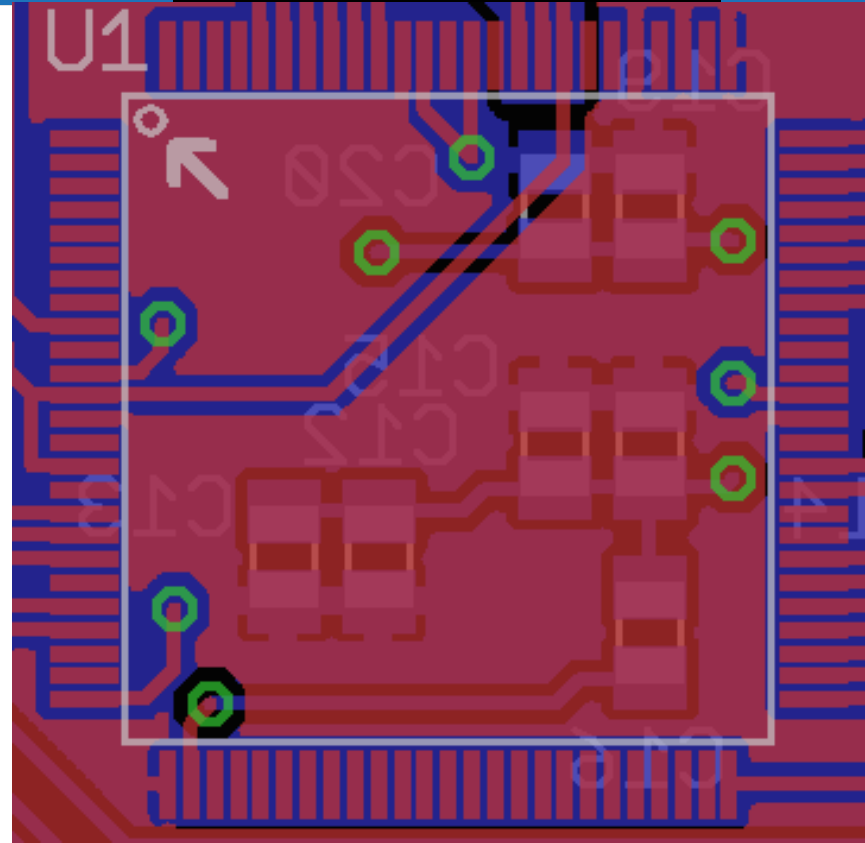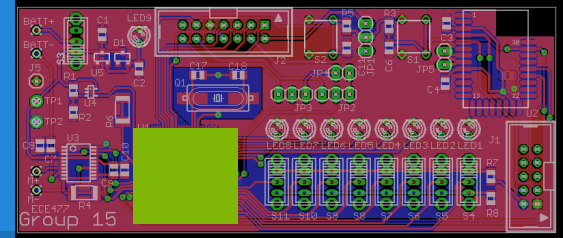


Bluetooth Layout

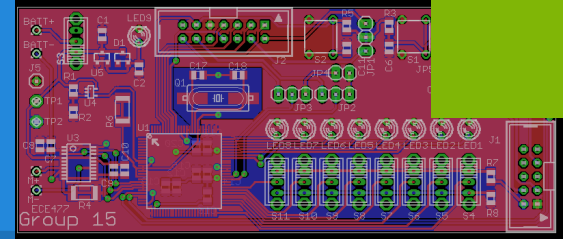


Signal planes
restricted near
antenna




Chip near corner for
minimal EMI




Debug UART header

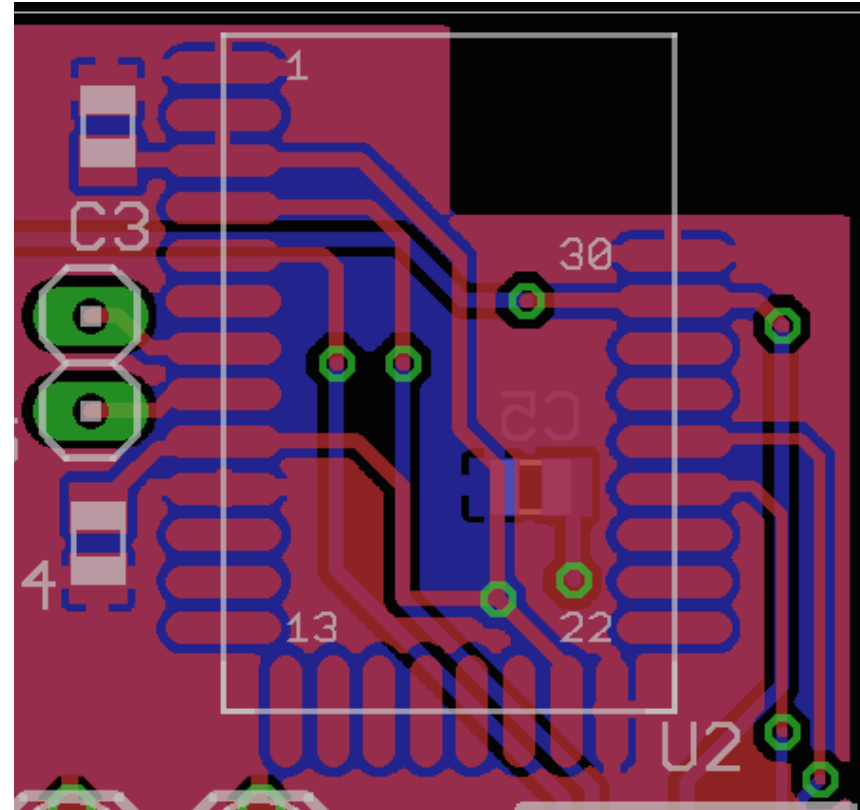


Software Structure and Status

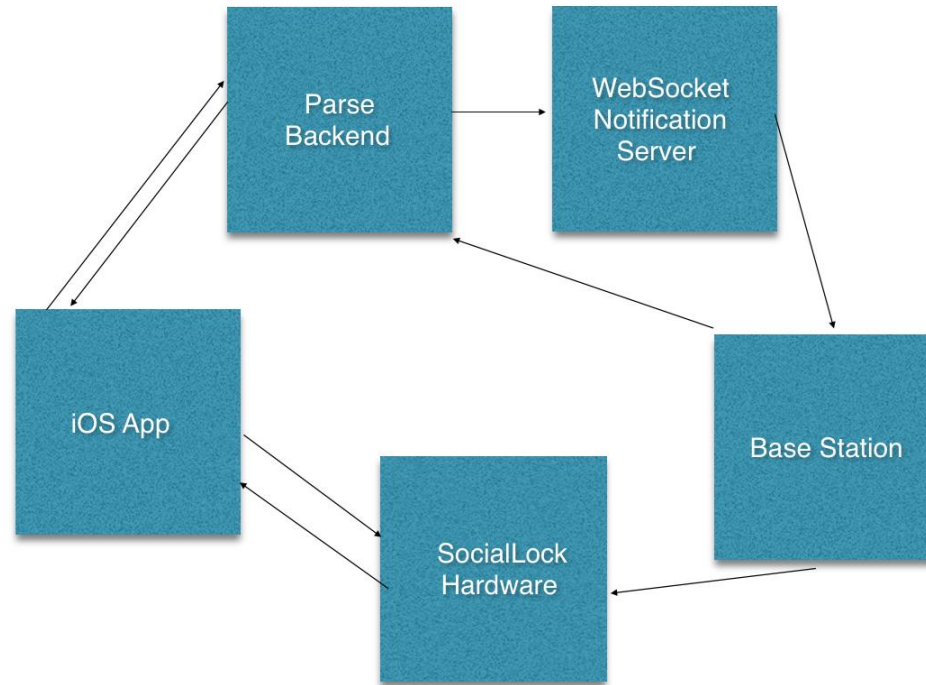

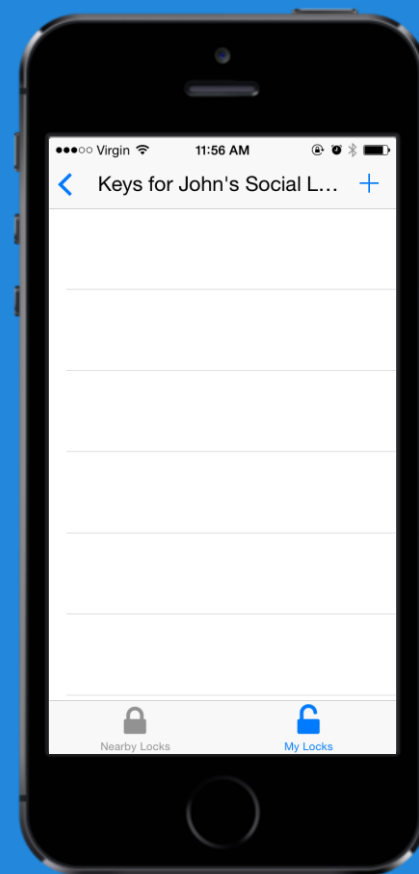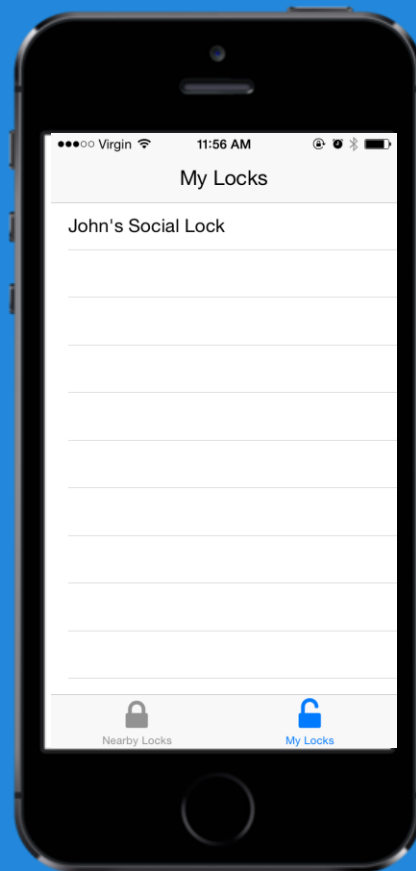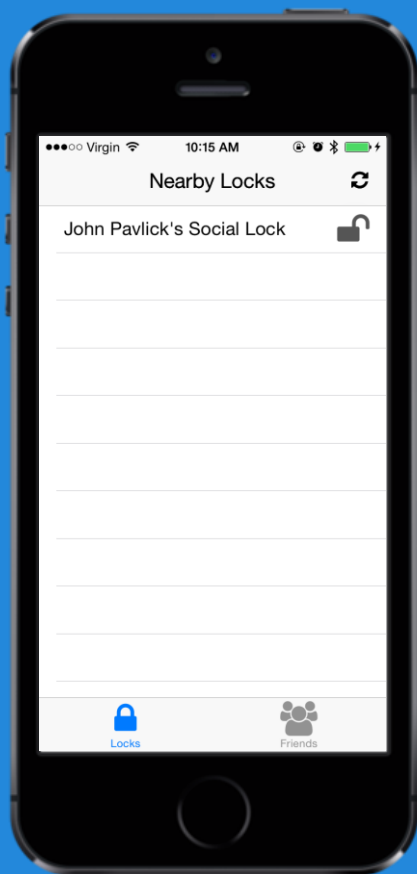

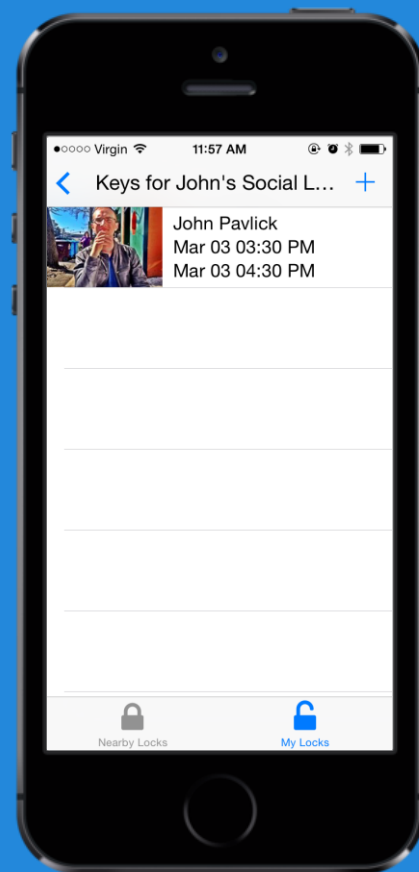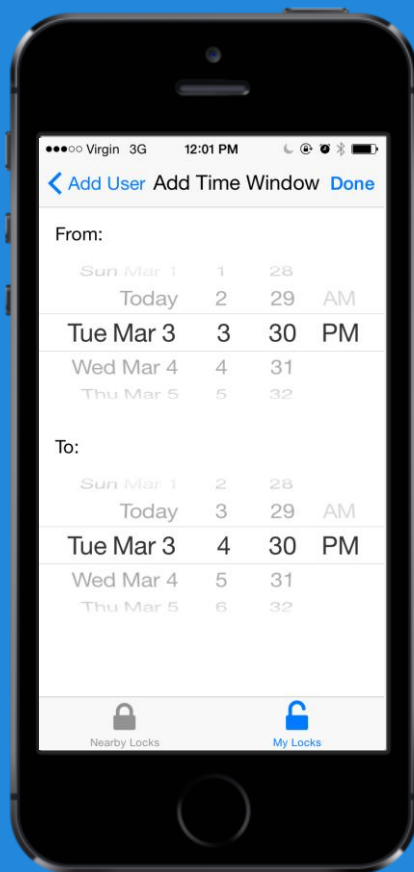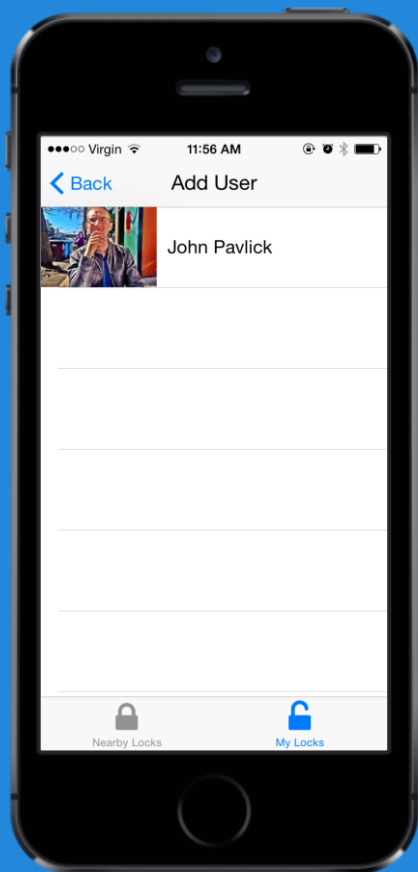


Software Structure and Status

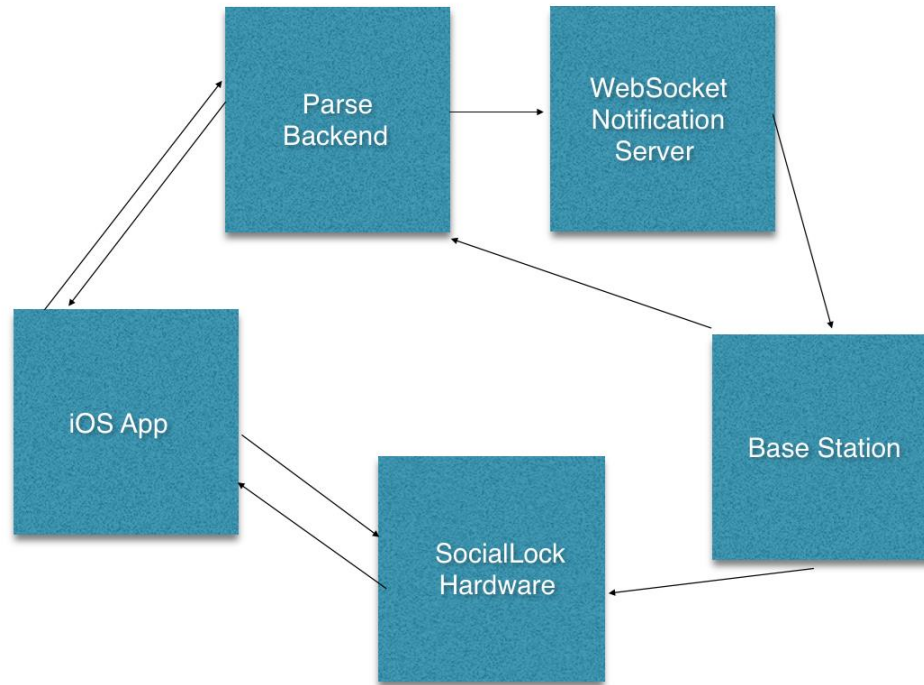


Software Structure and Status

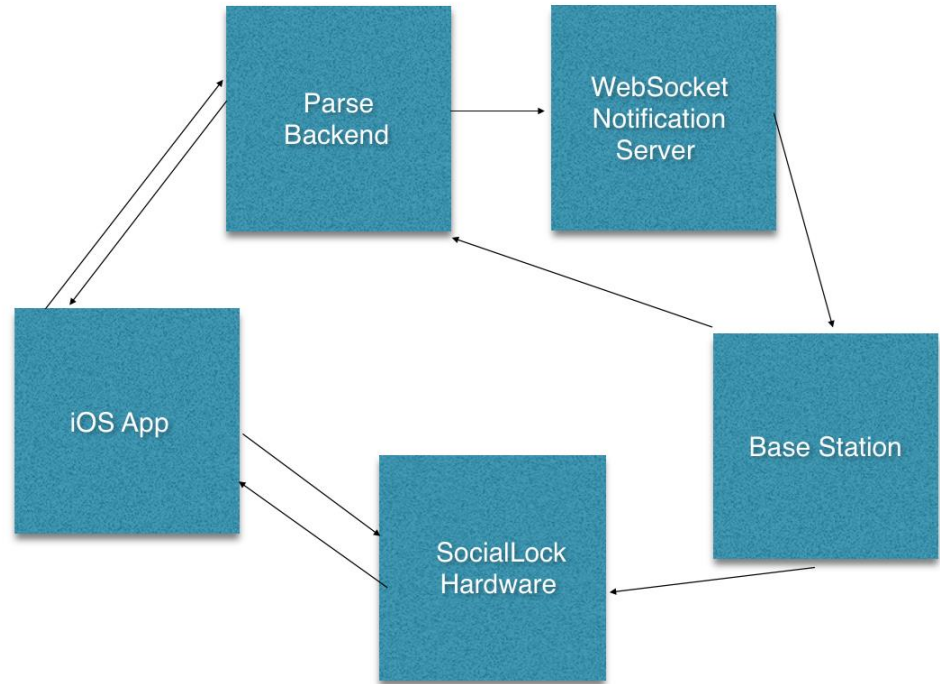- iOS App: Complete
- Parse Backend: Complete
- Base Station: Complete
- Bluetooth Chip: In Progress
- MSP430: In Progress



Project Completion Timeline

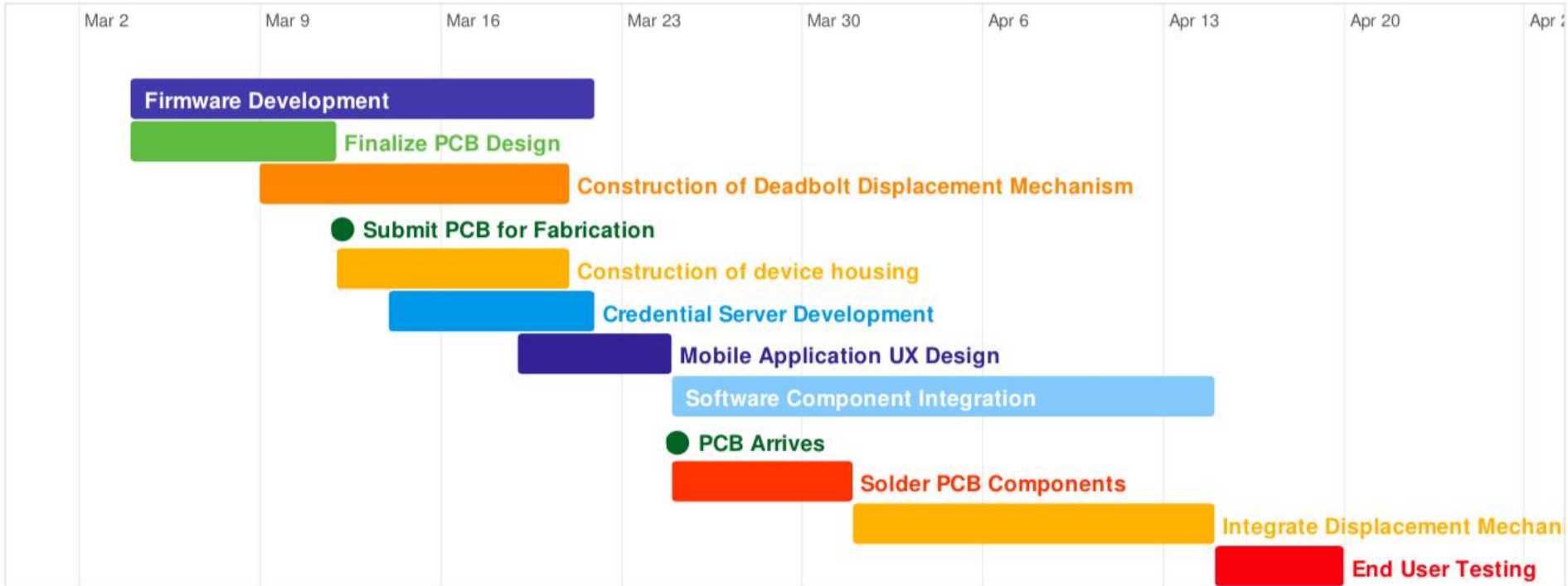

Questions?